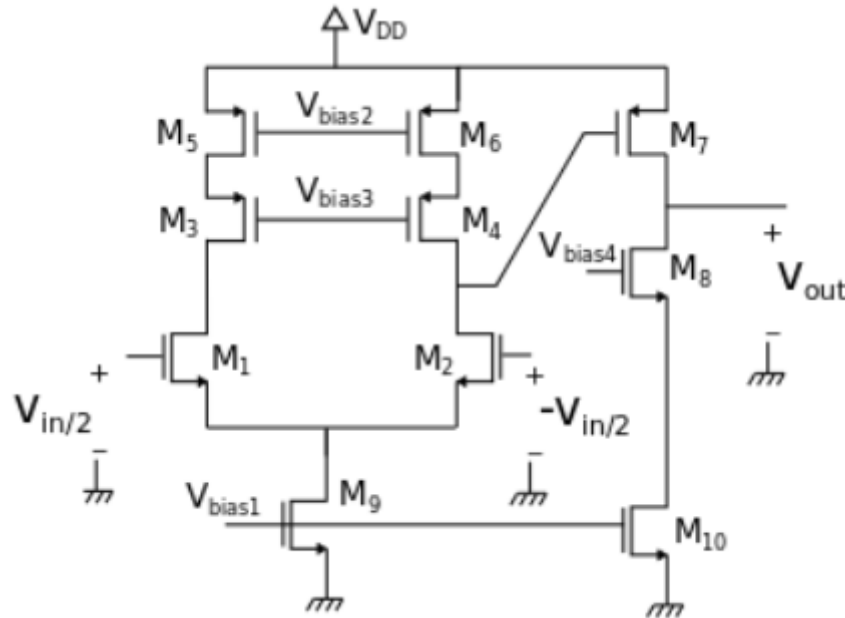



### Evaluation Test III

1. Given the following opamp, what is the gain  $V_{out}/V_{in}$ ? Assume that all the transistors are working in saturation, with  $(W/L)_1 = (W/L)_2$ ,  $(W/L)_3 = (W/L)_4$ , y  $(W/L)_5 = (W/L)_6$ .





- $-0.5 \cdot g_{m2} \cdot ((g_{m4} \cdot r_{ds4} \cdot r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (g_{m8} \cdot r_{ds8} \cdot r_{ds10}))$
  - $0.5 \cdot g_{m2} \cdot ((r_{ds4} + r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (r_{ds8} + r_{ds10}))$
  - $0.5 \cdot g_{m2} \cdot ((g_{m4} \cdot r_{ds4} \cdot r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (g_{m8} \cdot r_{ds8} \cdot r_{ds10}))$
  - $-0.5 \cdot g_{m2} \cdot ((r_{ds4} + r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (r_{ds8} + r_{ds10}))$
2. To design a flash converter a Miller opamp will be reused to make it work as a comparator. Which tasks should be done firstly?
- Redesign the values of the capacitor and the resistors used for compensation.
  - Remove compensation because comparators do not need to be compensated.
  - A Miller opamp cannot be used as a comparator.
  - Add an output stage with a common-drain configuration to achieve a high output resistance.

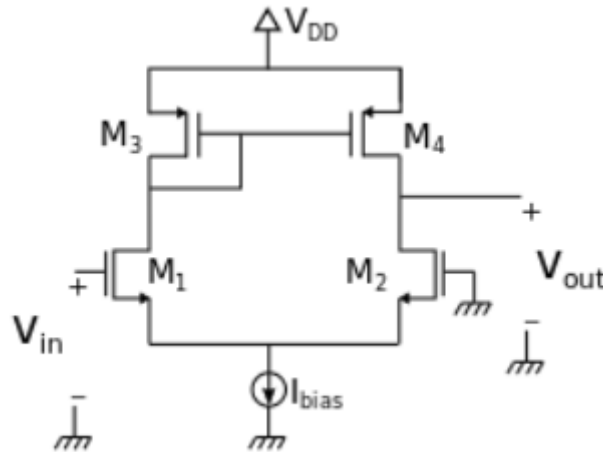3. The following comparator has been designed, where  $v_{in}$  is the input signal, and  $v_{out}$  is the output signal. Gain and delay time requirements are accomplished. If the maximum achievable output voltage must be increased, what could be done? Neglect potential penalizations over other requirements.



- Either reduce  $(W/L)_4$  or  $I_{bias}$ .
- Either reduce  $(W/L)_4$  or increase  $I_{bias}$ .
- Either increase  $(W/L)_4$  or reduce  $I_{bias}$ .
- Either increase  $(W/L)_4$  or  $I_{bias}$ .
- Any of the answers above is correct.


4. Given the following circuits:

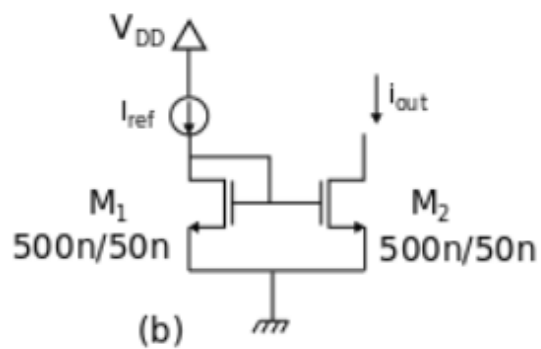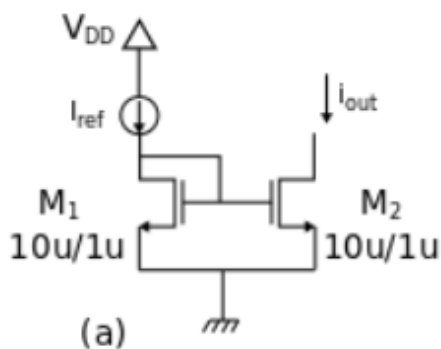

Which one has a higher output resistance?

- (a).
- (b).
- Both have the same output resistance.
- With the provided data it is not possible to know it.

5. Given the following circuits:

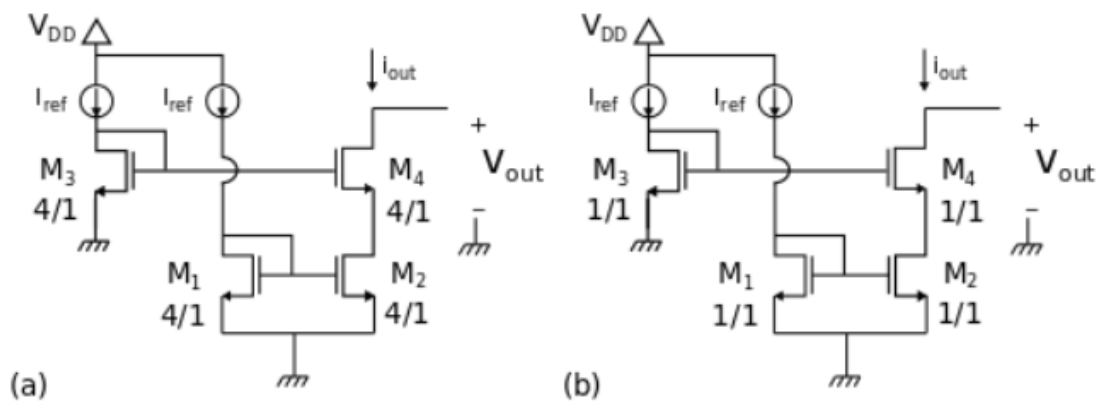

Which one has a lower value for  $V_{out}$  to ensure that all the transistors are working in saturation?

- a)  $V_{out,min,(a)}$  equals  $V_{out,min,(b)}$ .
- b)  $V_{out,min,(b)}$  is lower than  $V_{out,min,(a)}$  because  $V_{out,min,(a)}=16V_{out,min,(b)}$ .
- c)  $V_{out,min,(a)}$  is lower than  $V_{out,min,(b)}$  because  $V_{out,min,(b)}=16V_{out,min,(a)}$ .
- d)  $V_{out,min,(b)}$  is lower than  $V_{out,min,(a)}$  because  $V_{out,min,(a)}=2V_{out,min,(b)}$ .
- e)  $V_{out,min,(a)}$  is lower than  $V_{out,min,(b)}$  because  $V_{out,min,(b)}=2V_{out,min,(a)}$ .