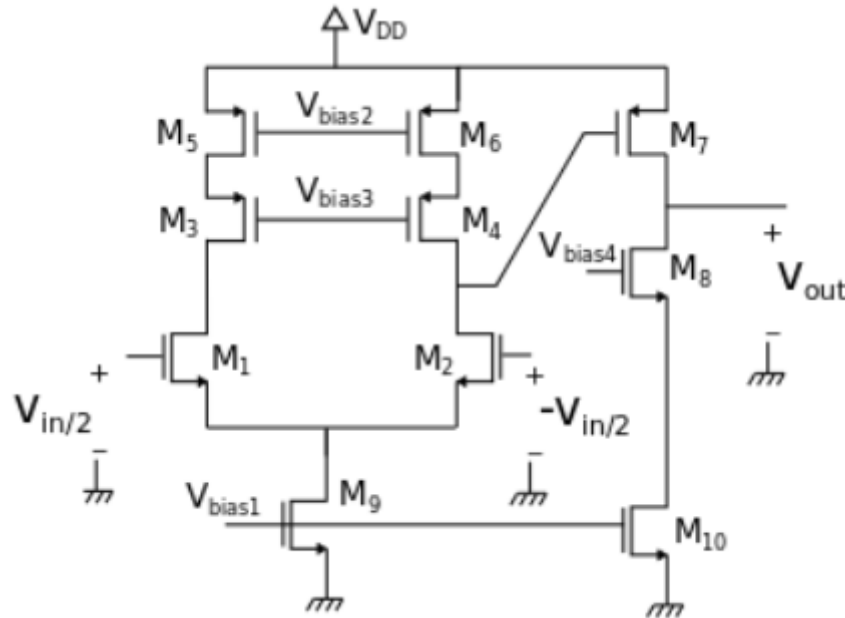


Evaluation Test III

1. Given the following opamp, what is the gain V_{out}/V_{in} ? Assume that all the transistors are working in saturation, with $(W/L)_1 = (W/L)_2$, $(W/L)_3 = (W/L)_4$, y $(W/L)_5 = (W/L)_6$.




- a) $-0.5 \cdot g_{m2} \cdot ((g_{m4} \cdot r_{ds4} \cdot r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (g_{m8} \cdot r_{ds8} \cdot r_{ds10}))$
- b) $0.5 \cdot g_{m2} \cdot ((r_{ds4} + r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (r_{ds8} + r_{ds10}))$
- c) $0.5 \cdot g_{m2} \cdot ((g_{m4} \cdot r_{ds4} \cdot r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (g_{m8} \cdot r_{ds8} \cdot r_{ds10}))$
- d) $-0.5 \cdot g_{m2} \cdot ((r_{ds4} + r_{ds6}) \parallel (r_{ds2})) \cdot g_{m7} \cdot ((r_{ds7}) \parallel (r_{ds8} + r_{ds10}))$

2. To design a flash converter a Miller opamp will be reused to make it work as a comparator. Which tasks should be done firstly?



- a) Redesign the values of the capacitor and the resistors used for compensation.
- b) Remove compensation because comparators do not need to be compensated.
- c) A Miller opamp cannot be used as a comparator.
- d) Add an output stage with a common-drain configuration to achieve a high output resistance.

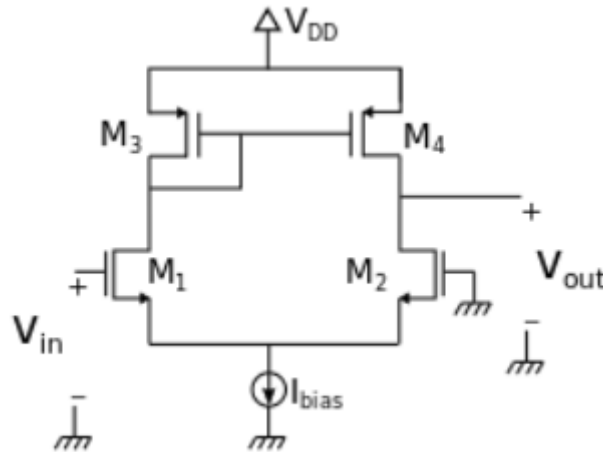3. The following comparator has been designed, where v_{in} is the input signal, and v_{out} is the output signal. Gain and delay time requirements are accomplished. If the maximum achievable output voltage must be increased, what could be done? Neglect potential penalizations over other requirements.



- Either reduce $(W/L)_4$ or I_{bias} .
- Either reduce $(W/L)_4$ or increase I_{bias} .
- Either increase $(W/L)_4$ or reduce I_{bias} .
- Either increase $(W/L)_4$ or I_{bias} .
- Any of the answers above is correct.


4. Given the following circuits:

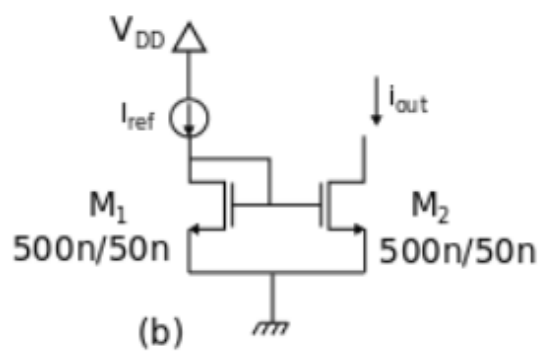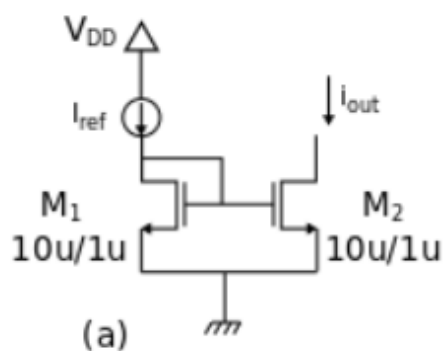

Which one has a higher output resistance?

- (a).
- (b).
- Both have the same output resistance.
- With the provided data it is not possible to know it.

5. Given the following circuits:

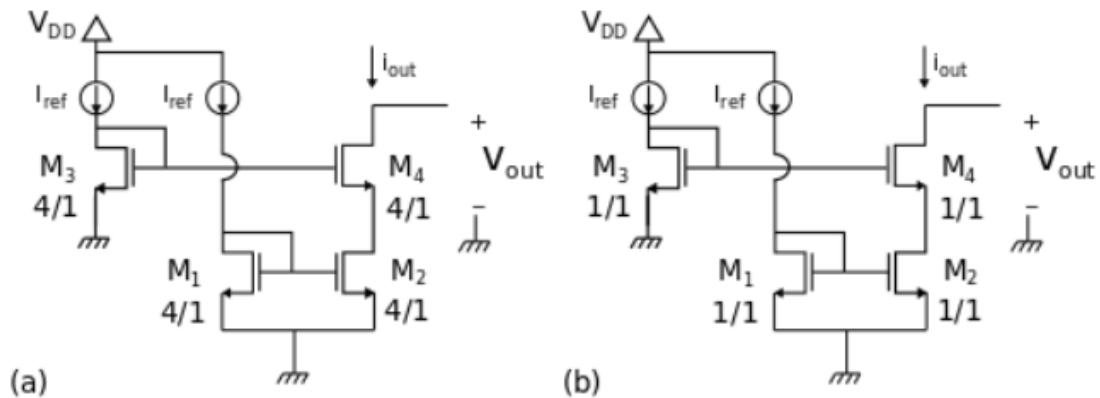

Which one has a lower value for V_{out} to ensure that all the transistors are working in saturation?

- a) $V_{out,min,(a)}$ equals $V_{out,min,(b)}$.
- b) $V_{out,min,(b)}$ is lower than $V_{out,min,(a)}$ because $V_{out,min,(a)}=16V_{out,min,(b)}$.
- c) $V_{out,min,(a)}$ is lower than $V_{out,min,(b)}$ because $V_{out,min,(b)}=16V_{out,min,(a)}$.
- d) $V_{out,min,(b)}$ is lower than $V_{out,min,(a)}$ because $V_{out,min,(a)}=2V_{out,min,(b)}$.
- e) $V_{out,min,(a)}$ is lower than $V_{out,min,(b)}$ because $V_{out,min,(b)}=2V_{out,min,(a)}$.