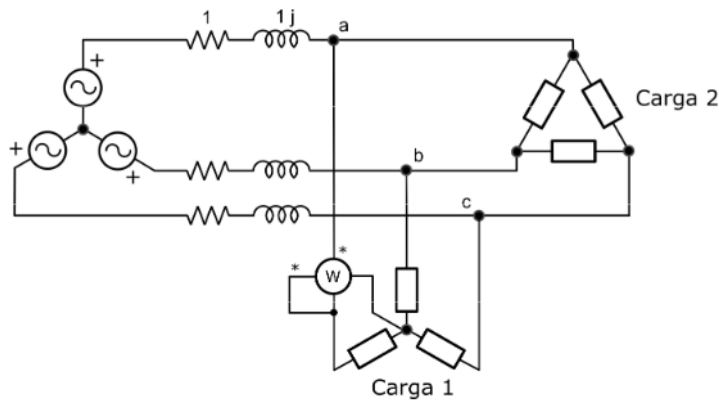


Examen 11 enero 2018 - Trifásica.



$$V_g = 350,9 < 14,09^\circ$$

$$I_1 = 55,9 \text{ A}$$


$$P_1 = 18750 \text{ W}$$

$$\cos\varphi_1 = 0,477$$

$$Z_2 = 18 - 6j\Omega$$

Impedancia Z_1 ; $P_1 = 3 \cdot I_1^2 \cdot R_1$; $\varphi_1 = \arccos 0,477 = 63,45^\circ$
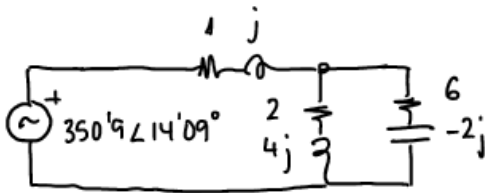
$$R_1 = \frac{18750}{3 \cdot 55,9^2} = 2\Omega; X_1 = R_1 \tan\varphi_1 = 4\Omega \quad \text{Entonces } Z_1 = 2 + 4j\Omega$$



$$\frac{V_a - 350,9 < 14,09}{1+j} + \frac{V_a}{2+4j} + \frac{V_a}{6-2j} = 0$$

$$V_a \left(\frac{1}{1+j} + \frac{1}{2+4j} + \frac{1}{6-2j} \right) = \frac{350,9 < 14,09}{1+j}$$


$$V_a = \frac{248,12 < -30,9}{0,99 < -40,9} = 250 < 10^\circ \text{ V}$$

$$S_g = 3V_F I_F^*$$

$$I = \frac{350,9 < 14,09 - 250 < 10}{1+j} = 72,9 < -20,95^\circ \text{ A}; S_g = 3 \cdot 350,9 < 14,09 \cdot 72,9 < 20,95$$

$$S_g = 76737,6 < 35^\circ = 62829,1 + 44058,6j \text{ VA}$$

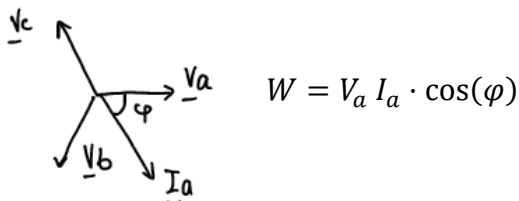El vatímetro mide $\frac{P}{3} = 6250 \text{ W}$



$$W = V_a I_a \cdot \cos(\varphi)$$

$$I_1 = \frac{250 < 10}{2+4j} = 55,9 < -53,43^\circ \text{ A}$$

$$I_2 = \frac{250 \angle 10}{6 - 2j} = 39,53 \angle 28,43^\circ \text{ A}$$

$$P = P_1 + P_2 = 18750 + 28127,2 = 46877,2 \text{ W}$$

$$P = 3 \cdot 39,53^2 \cdot 6 = 28127,2 \text{ W}$$

$$\varphi = \varphi_v - \varphi_i = 10 - (-20,95) = 31^\circ$$

$$C_\Delta = \frac{46877,2}{3} \cdot \frac{\text{tg}31}{(250 \cdot \sqrt{3})^2 \cdot 100\pi} = 159,4 \mu\text{F}$$

$\cos \varphi = \cos 31 = 0,857$ Con un factor de potencia de 0,857 no sería necesario compensar reactiva.

$$P' = 3 \cdot V_F I'_F \cdot \cos \varphi' \rightarrow \frac{46877,2}{3 \cdot 250} = I' = 62,5 \therefore 72,9 \text{ A}$$

